

Edited by Bill Travis and Anne Watson Swager

Fast algorithm computes histograms

Lukasz Sliwczynski, University of Mining and Metallurgy, Cracow, Poland

A HISTOGRAM IS A convenient method of presenting statistical features of data; you can use a histogram for an estimate of the probability density function of a random phenomenon. To prepare a histogram entails dividing the interval occupied by data values into some number of smaller intervals and then counting the number of occurrences of data in each subinterval. You can easily generate histograms with the aid of standard mathematical packages, such as Matlab. The problem lies in the fact that calculating a histogram using the standard Matlab function `hist()` from a large file of data (for example, 10 million data points) with high accuracy (for example, with 12-bit resolution) may take substantial time—many hours, or even days, depending on computer speed and memory. The problem is that `hist()` treats its input data as “analog” data with almost infinite precision, and the routine must use program loops, which are very slow in Matlab.

However, you often perform measure-

LISTING 1—MATLAB PROGRAM FOR FAST HISTOGRAM CALCULATION


```
function N=fasthist(g,L,W)
%
% N=fasthist(g,L,W)
%
% Function calculates histogram of data from D/A converter.
% Range of numbers is from 0 to 2^L. Subinterval length is W.
% L is the number of bits of the converter.

g=g(:);
gs=sort(g);
gsd=diff(gs);
index=find(gsd);
V=[gs(index),gs(length(gsd))+1];
N=zeros(1,2^L);
N(V)=1;
if W~=1
    for i=1:fix(2^L/W)
        N(i)=sum(N(W*(i-1)+1:W*i));
    end;
end;
N=N(1:fix(2^L/W));
```

ments with the use of A/D conversion, with the result that the input data for the histogram-calculating procedure are discrete and that the smallest difference between any two data values is one. This fact allows you to write a special function for calculating the histogram. You can use the complete Matlab program for calculating histograms from discrete data (Listing 1). The program is intended for placement into a Matlab m-file, which creates a function from the routine. This function is acces-

sible from the Matlab command window, just as any other function. Figure 1 illus-

Figure 1

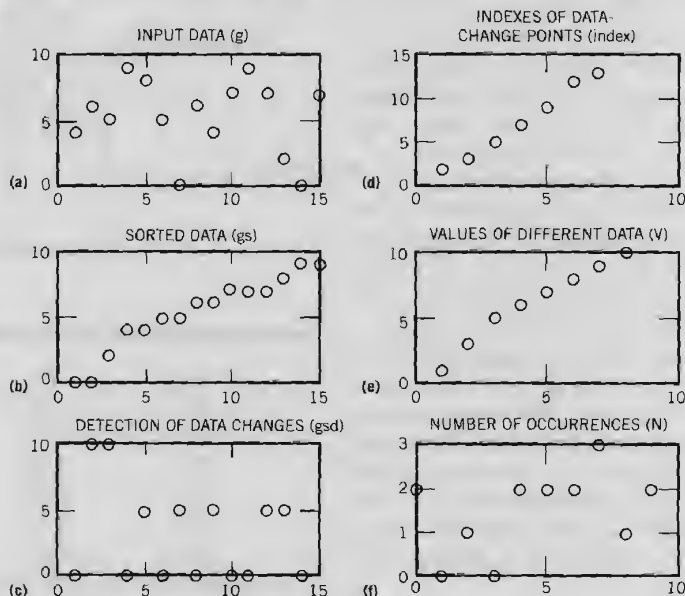

Ordering of the data points in diagrams a through f follows the steps in Listing 1.

Fast algorithm computes histograms	151
Loop powers current transmitter	152
Spice creates time-variant resistor	154
VCO supply touts low noise	154
μC forms FM oscillator	158
Circuit converts pulse width to voltage	160
Restore dc to NRZ signals	162

trates the operation of the algorithm. The first line (1) of the program prepares input data and gives the data the form of the column vector *g* (Figure 1a). The second line (2) performs data sorting and arranges the data in ascending order (*gs* in Figure 1b). The difference vector *gsd* in Figure 1c has peaks only at those points where data changes; elsewhere, the vector has a value of zero. The distance between two consecutive peaks is equal to the number of data samples of the same values, and the height of a peak is equal to the distance between two consecutive numbers.

Next, the routine (4) calculates the indexes of data changes (Figure 1d) and calculates the values of data *V* (Figure 1e) appearing in input vector *g* (5). A "1" in this code line is necessary because a vec-

tor index cannot equal zero in Matlab. In the following step (7), the step vector *V* indexes the output vector from the procedure *N*. This indexing operation is simple and fast because both indexes and data are natural numbers and belong to the same interval $[0; 2^L - 1]$. At this point, the essential part of the procedure is finished. The numbers *N*(*i*) (Figure 1f) are equal to the total number of occurrences of data with the value *i* - 1 in the input vector *g*. The last six lines of the program reduce the initial resolution of the A/D converter that you use to acquire data. To obtain faster execution of the program, you switch on this part of the routine only when necessary—for example, when *W* does not equal 1.

The effect of using this algorithm rather than the standard one in the Mat-

lab package is significant. Using the standard function *hist*{}, the time to compute a histogram from 10,000 points is 10 sec; for the same data file with 12-bit resolution, the algorithm *fasthist*{}, requires only 0.55 sec. These figures are based on using a 100-MHz Pentium machine with 33 Mbytes of RAM, running under Windows 95. Using *fasthist*{}, a histogram from a 10 million-point data file takes approximately a half-hour as opposed to more than a day using *hist*{}. These results occur using Matlab version 4.2. Version 5.2 gives somewhat different results: 68 sec for *hist*{}, and 0.38 sec for *fasthist*{}, a 179-times reduction. (DI #2422)

TO VOTE FOR THIS DESIGN,
CIRCLE No. 358

Loop powers current transmitter

By N Kannan, Mediatronix Ltd, Triandrum, India

IN THE CIRCUIT in Figure 1, the loop supply is 20 to 30V dc, and the loop current is 10 to 20 mA. *IC*₁ operates as a constant-current (*I*_p) source. *IC*₂, *R*₁, and *R*₂ operate as a shunt regulator, which provides 12V *V*_{CC}. *IC*₂ is a TLO32 op amp. The sensor circuit could be a resistance-temperature-detector circuit or any other sensor- or signal-conditioning circuit. The *IC*₂/*Q*₁ combination operates as a current sink, with *I*_C = *V*_{IN}/*R*_E. The total loop current is *I*_p + *I*_C. Because of its common-mode input-range limitation, *IC*₂ requires a minimum 2V input for proper operation. Hence, the *V*_{IN} signal range must be 2 to 10V. With *V*_{IN} = 2V, you adjust potentiometer *P*₁ to set *I*_{LOOP} at 10 mA. At this operating point, *I*_C = 4 mA, and the balance of the current (*I*_p = 6 mA) goes to the shunt regulator, the op amp, and the sensor-circuit load. The maximum load current is typically 5 mA. As *V*_{IN} increases from 2 to 10V, *I*_{LOOP} increases proportionally, solely from the increase in *I*_p, because *I*_C is constant:

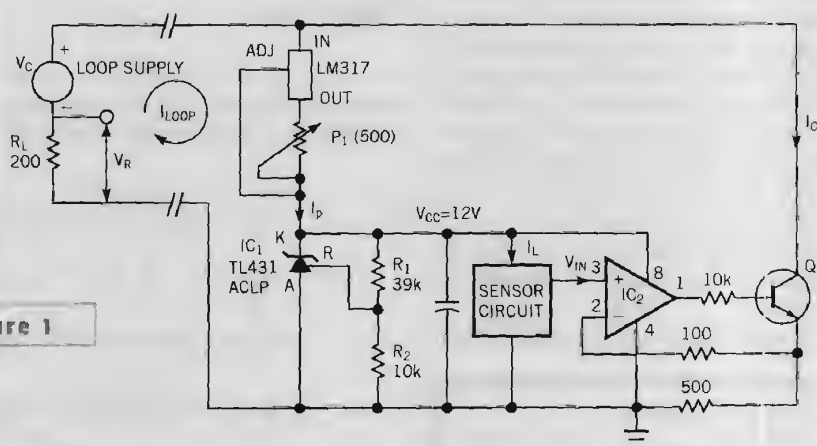


Figure 1

Inexpensive components provide an efficient loop-powered current transmitter.

<i>V</i> _{IN}	<i>V</i> _R
2V	2V
3V	2.4V
4V	2.8V
6V	3.6V
8V	4.4V
10V	5.2V

For every 1V increase in *V*_{IN}, the change in *V*_R is 0.4V. The circuit has good

accuracy and temperature stability and operates with loop supplies of 20 to 30V. The maximum available sensor-circuit current is approximately 5 mA. Currents greater than this value result in poor *V*_{CC} regulation. (DI #2421).

TO VOTE FOR THIS DESIGN,
CIRCLE No. 359

Spice creates time-variant resistor

Vittorio Ricchiuti, Italtel, L'Aquila, Italy


FIGURE 1 SHOWS A SUBCIRCUIT that represents the behavioral model of a linearly time-variant resistor in PSpice (Orcad, www.orcad.com). PSpice libraries include no models of such resistors, which you can use in various applications—for example, to simulate the fallback characteristic of a linear regulator in transient analysis. The suggested model uses the E-device in the PSpice analog-behavioral-modeling parts library. Listing 1 describes the subcircuit in Figure 1 for a time-variant resistor with the characteristic in Figure 2. The function in Figure 2 is the product of an independent voltage source, V_{CONTROL} . The independent zero-voltage source V_{SENSE} senses the current $I(V_{\text{SENSE}})$ through the resistor. The voltage V_R between nodes 1 and 2 of the time-variant resistor is $V_R = f(t) * I(V_{\text{SENSE}})$, where $f(t)$ is a function of V_{CONTROL} . (DI #2424)

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 360

LISTING 1—MACRO MODEL OF TIME-VARIANT RESISTOR

```
*
SUBCKT VAR_RES 1 2
R_R1 0 4 1G
V_Vcontrol 4 0
+PWL 2n 1k 4n 0 6n 1k
*
E_Res_lin 3 2 VALUE { I(V_Vsense)*V(4, 0) }
*
V_Vsense 1 3 DC 0V AC 0V 0V
*
.ENDS VAR_RES
```

Figure 1

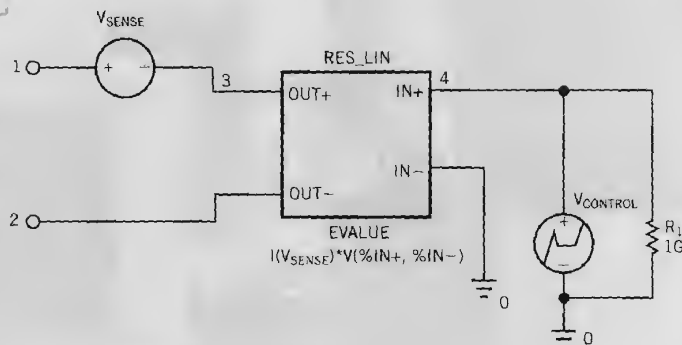

A subcircuit provides the behavioral model of a time-variant resistor.

Figure 2



The routine in Listing 1 simulates a linearly time-variant resistor.

VCO supply touts low noise


Ted Henderson, Linear Technology Corp, Milpitas, CA

MANY PORTABLE RF PRODUCTS use VCOs to generate the RF carrier frequency. These applications often require low-noise VCO power-supply

voltages that are higher than the primary battery voltage. Many designs use a dc/dc converter powering a low-noise linear regulator. This approach has several in-

herent disadvantages. The dc/dc converter produces noise that the regulator may not reject, resulting in regulator-output noise far greater than the thermal-noise

Figure 1

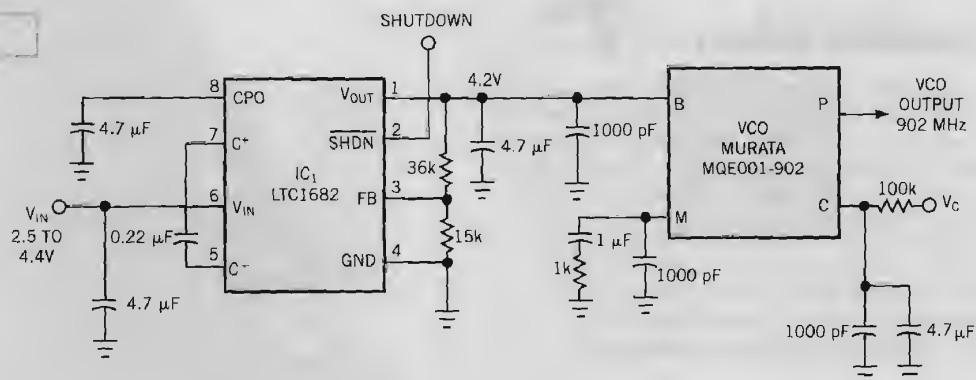


A single IC can generate a low-noise voltage for controlling a VCO.

levels. The linear regulator might require a large output-compensation capacitor with stringent ESR requirements. Finally, the board area for both devices and support components can be large. The circuit in **Figure 1** operates from an input range of 2.5 to 4.4V and generates a 4.2V low-noise voltage for a 900-MHz VCO.

The circuit is based on IC₁, an LTC1682 charge-pump dc/dc converter. The device includes a charge-pump/linear-regulator tandem that's optimized for minimum regulator-output noise. The linear regulator operates with several types of output capacitors, including small, low-value, low-ESR ceramic capacitors. **Figure 2** shows the close-in phase noise of the VCO operating in open-loop mode; **Figure 3** shows the peak-to-peak noise voltage at the regulator's output. (DI #2430).

Figure 2


AMPLITUDE
(10 dB/DIV)

 

The VCO in Figure 1 exhibits low close-in phase noise.

Figure 3

V_{OUT}
(200 µV/DIV)

 

100 µSEC/DIV

The supply in Figure 1 generates only approximately 200 mV of peak-to-peak noise.

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 361

μC forms FM oscillator

Abel Raynus, Armatron International, Melrose, MA

A PROJECT REQUIRED AN inexpensive oscillator whose frequency increased step by step from 200 to 400 Hz and then decreased to 200 Hz. The first step was to design a VCO with a staircase driver. However, this approach entailed at least four ICs and many discrete components. An alternative method (Figure 1) requires only one 16-pin μC (an MC68HC705KJ1, costing less than \$1) and only a few external components. The process takes place exclusively in software (Listing 1). The μC generates a burst of 256 cycles of a given period. After that, the period decrements or increments, and the μC generates a burst with the new period. The choice of decrement or increment depends on the contents of the flag register. If the flag is zero, it is a sign to decrement; otherwise, to increment. When the set of frequencies reaches completion, the content of the register inverts. So, in one operation, the frequencies grow; in the next, they decrease.

Keep in mind that a linear change in the value of the period causes a nonlinear change in the frequency value (according to a hyperbolic curve). So, you should perform all calculations in the

time domain, rather than in the frequency domain. In our application, the nonlinear aspect of the frequency is unimportant. However, if necessary, you can realize any kind of FM by organizing the table of frequencies corresponding to each step. The design determines the pe-

riod resolution, ΔT . In this case, it equals 0.02 msec, because this value allows you to use only one 8-bit register (HPER) to perform all period-changing operations

For more precision, you could use two or more registers. The number of frequencies in the set is $K2_{MAX} = (T_{MAX} -$


LISTING 1—μC ASSEMBLY CODE FOR FREQUENCY GENERATOR

```

1  * Quasy FM Oscillator
2  * range 200 Hz - 400 Hz,
3  * period discretion - 0.02 ms
4  * number of frequencies - 125
5  *****
6  *nolist
7  $include "std-jla.asm"
8  *list
9  *I/O PORTS
10 out equ 7;prta pin11
11 *CONSTANTS
12 HPmax equ 250T; frequency = 200 Hz
13 *VARIABLES
14 org RAM
15 k1 rmb 1 ;sound duration counter
16 k2 rmb 1 ;frequency number counter
17 HPER rmb 1 ;Half of Period register
18 flag rmb 1 ;flag register
19 *INITIALIZATION
20 org MOR
21 fcb %00100000 ;Osc.parall.resistor
22 org ROM
23 init lda #fff
24 sta ddrA ;set prta for output
25 clr k1 ;0 -> k1
26 clr k2 ;0 -> k2
27 clr flag
28 lda #HPmax
29 sta HPER ;set T = 5 ms, f = 200 kHz
30 main jsr burst; generate 256 cycles
31 tst flag
32 beq m1
33 inc HPER ; HPER + 1
34 inc k2 ; k2 + 1
35 lda k2 ; k2 -> ACC
36 cmp #125T; k2 < 125?
37 blo main
38 lda flag ;inverting flag
39 eor #1 ;
40 sta flag ;
41 clr k2 ; 0 -> k2
42 bra main
43 m1 dec HPER ;HPER - 1
44 bra m2
45 burst bset out,prta ;1 -> out
46 ldx HPER ;HPER -> x
47 jsr dly01x ;half period delay
48 bclr out,prta ;0 -> out
49 ldx HPER ;HPER -> x
50 jsr dly01x ;half period delay
51 inc k1 ;k1 + 1
52 tst k1 ;k1 = 0?
53 bne burst
54 rts ;return from burst
55 dly01x lda #2 ;delay 0.01x ms
56 rep0 decA
57 bne rep0
58 decx
59 bne dly01x
60 rts ;return from dly01x
61 *****
62 org VECTORS+6
63 fcb init

```

Figure 1

 

An inexpensive μC replaces complicated VCO circuitry to configure a simple frequency-step generator.

$T_{MIN})/\Delta T$. You can determine any frequency is the set as:

$$\text{Flag}=0; f_K=1/(T_{MAX}-\Delta T \cdot K2).$$

$$\text{Flag}=1; f_K=1/(T_{MIN}+\Delta T \cdot K2).$$

Table 1 shows some of the frequencies. The duration of the set is $t = 1/2(T_{MAX}+T_{MIN}) \cdot K1_{MAX} \cdot K2_{MAX}$. In this case, $t=2$ msec (DI #2432).

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 362

TABLE 1—200- TO 400-Hz FREQUENCY STEPS

Flag	K2	T (msec)	1/2T (msec)	HPER	F (Hz)	Comments
0	0	5.00	2.50	250	200.0	T_{MAX}
0	1	4.98	2.49	249	200.8	
0	2	4.96	2.48	248	201.6	
0	3	4.94	2.47	247	202.4	
...	
0	123	2.54	1.27	127	393.7	T_{MIN}
0	124	2.52	1.26	126	396.8	
0	0	2.50	1.25	125	400.0	
1	1	2.52	1.26	126	396.8	
1	2	2.54	1.27	127	393.7	
1	3	2.56	1.28	128	390.6	


Circuit converts pulse width to voltage

Ron Hegler, Picker International, Cleveland, OH

THE CIRCUIT IN Figure 1 stems from a radio-controlled modeling ap-

Figure 1

plication, which requires a voltage proportional to the width of the incoming servo pulses. The circuit is optimized for a positive-going pulse width of 1 to 2 msec, repeating at intervals of approximately 17 msec. The output produces a voltage of 0.95V for a 1-msec pulse to 2.25V for a 2-msec pulse. The circuit operates similarly to a PLL, but it locks onto the pulse width, rather than to the frequency, of the incoming signal. IC_{1A} is a one-shot multivibrator with its time constant a function of R_1 , the FET's on-resistance, and C_1 . IC_{1B} is a pulse-width comparator that compares the reference pulse from IC_{1A} with the incoming pulse. Upon the rise of the incoming pulse, IC_{1A} 's Q output clocks high and drives IC_{1B} 's D input high. If IC_{1A} times out before the input pulse falls, IC_{1A} 's Q output goes low, driving the D input of IC_{1B} low. This action drives the \bar{Q} of IC_{1B} high when the input pulse falls. The \bar{Q}

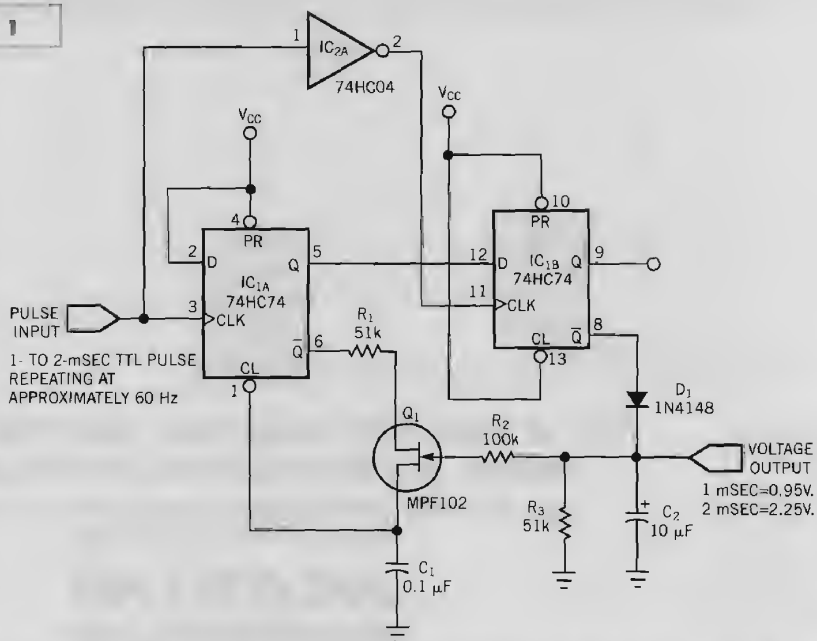

This pulse-width-locked loop provides an output voltage proportional to the incoming pulse width.

output connects to the FET through D_1 and R_2 . C_2 filters the \bar{Q} output to adjust the time constant of one-shot IC_{1A} to match the incoming pulse. The voltage

across C_2 indicates the incoming pulse width. (DI #2431).

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 363


Restore dc to NRZ signals

Jay Kirschenbaum, Columbia University, New York, NY

FOR NRZ SIGNALS, ac amplification is preferable to dc amplification, because ac amplification is usually more economical and has greater immunity to drift. However, ac processing has the disadvantage that ac coupling removes the dc reference level of the digital data stream. As **Figure 1** shows, if a long string of ones or zeros appears at the amplifier's input, the output droops after a period determined by the RC time constant at the input. This problem makes it necessary to include a dc-restoration circuit following the ac amplifier.

The circuit in **Figure 2** restores the dc level that the amplifier removes and eliminates droop, even if long strings of ones

Figure 1

 


A long string of ones or zeros leads to droop in a purely ac-coupled digital amplifier.

or zeros appear in the data stream. The circuit also provides additional amplification, increasing the signal to ECL levels.

Synchronous clocking gives the circuit good immunity to noise in the data channel. Tests reveal that the circuit op-

Figure 2

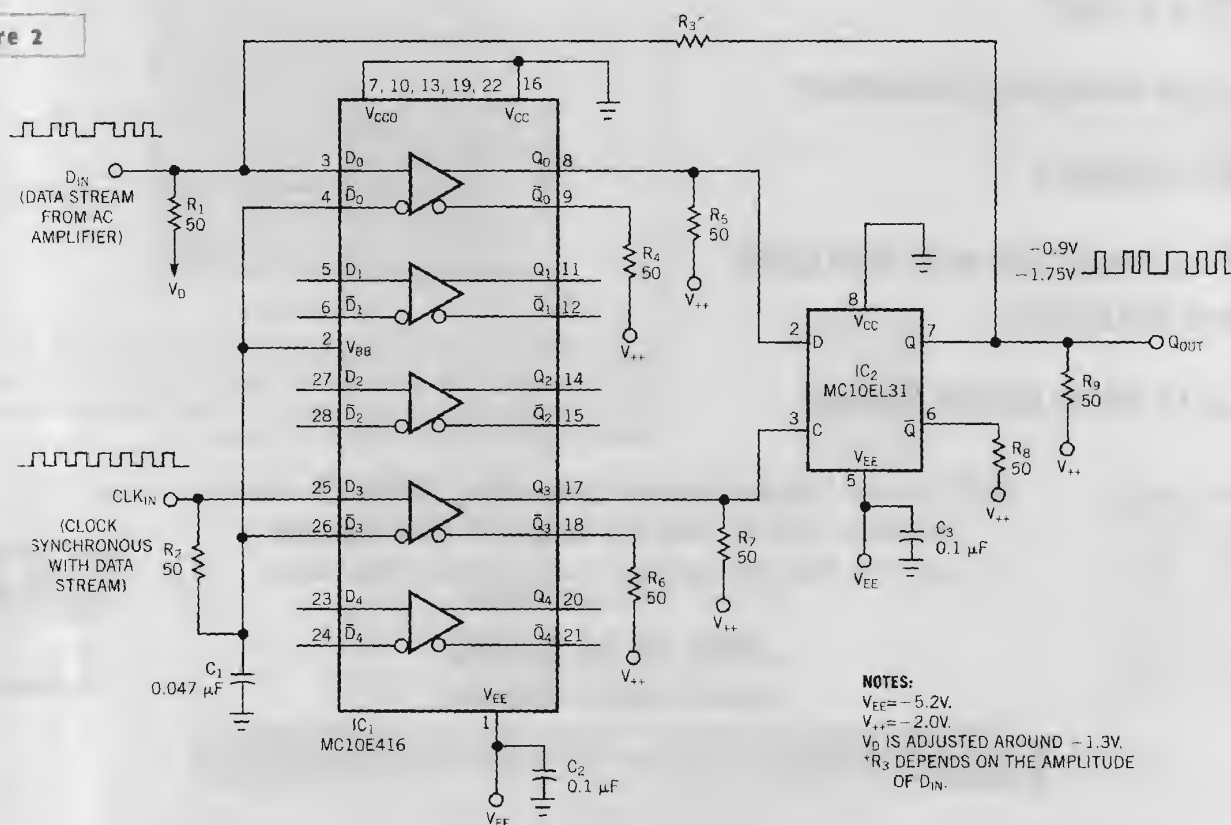

This circuit eliminates the droop from the data stream in Figure 1 and simultaneously amplifies the digital signal to ECL levels.

operates satisfactorily at clock speeds from dc to 1 GHz.

IC₁ is an MC10E416 five-channel line receiver, which boosts digital signals from a minimum of 50 mV p-p to ECL levels. The input circuit of each channel of IC₁ is a differential amplifier, which responds when the signal level at the true input swings past the signal at the complementary input. In Figure 2, the input data stream goes to the D₀ channel. The complementary input \bar{D}_0 connects to the V_{BB} pin, which is at -1.3V. The true input D₀ connects to bias voltage V_D through 50Ω. V_D is also nominally -1.3V, but you can tweak it to compensate for device characteristics. IC₂ is an MC10EL31 flip-flop. Both ICs are specified to 2 GHz. The logic level at D_{IN} transfers to Q_{OUT} at the positive transition of the signal at CLK_{IN}. Resistor R₃ and the 50Ω pull-down resistor, R_p, form a voltage divider that puts D₀ above or below $\sqrt{D_0}$ by half the expected input-voltage swing. The value of R₃ is a function of the swing of the input signal. For example,


assume D_{IN} has the value 100 mV p-p. If R₃ is 370Ω, and Q_{OUT} is at logic zero (-1.75V), the voltage divider sets D₀ 50 mV below \bar{D}_0 , and Q_{OUT} stays at logic zero as long as these conditions prevail.

Now suppose that logic one appears at D_{IN}. This condition simultaneously puts D₀ 50 mV above \bar{D}_0 , and Q_{OUT} switches to logic one (-0.9V) at the next clock transition. When this condition happens, the R₁-R₃ voltage divider holds D₀ 50 mV above \bar{D}_0 , and Q_{OUT} stays at logic one until the next transition to logic zero. Voltage droop disappears, and the dc reference of the digital signal re-establishes itself. Moreover, the circuit amplifies the 100-mV swing of the digital signal to ECL levels. Because the circuit triggers only when the clock edge appears, it's highly immune to noise in the data channel. At power-up, one transition from logic zero to logic one and one transition from logic one to logic zero are necessary at the amplifier input to put the circuit in a defined state. After that sequence, the circuit faithfully follows the input.

Proper timing between the data and the clock is important to reach the maximum operating speed of the circuit. Ideally, the clock edge should arrive at IC₁ as soon as the data-setup time is over, switching Q_{OUT} and pulling up D_{IN} as close to the data transition as possible. The theoretical upper limit on the operating (clock) frequency is a function of the propagation delay through the circuit (825 psec at 25°C). Data transitions must be spaced at least this far apart, so the maximum clock frequency is 1.2 GHz. Tests show that the circuit operates successfully at clock frequencies of dc to 1 GHz and data frequencies of dc to 500 MHz. The tests used a square wave for the clock input and a synchronous square wave of a lower frequency at the data input. The circuit restores the dc level and amplifies the signal to ECL levels over the entire test range. (DI #2434).

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 364

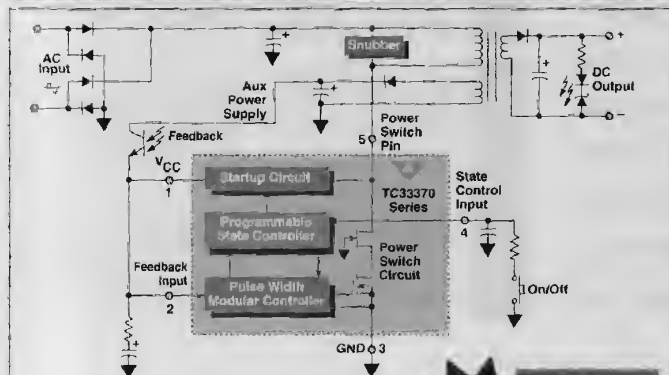TelCom Offers Highly Integrated, Very-High-Voltage Off-Line Switching Regulators that Simplify Your Power Converter Designs



TC33370 Series Applications

- Consumer Electronics
- Office Automation
- Personal Computers
- Wireless Communications
- Industrial Systems

Order
Your EV Kit
Today!



Device	Power Switch	
	On Resistance (Ω)	Peak Current (A)
TC33370	12	0.9
TC33371	6.8	1.5
TC33372	4.8	2.0
TC33373	3.8	2.7
TC33374	3.0	3.3

TC33370 Series Features

- Simplified Interface allows On/Off Control by a Microcontroller or other Circuitry
- Lower System Cost with Reduced Component Count for a Total Converter System Solution
- Improved Reliability with Internal Thermal Shutdown Protection, Cycle-by-Cycle Current Limiting, and Input Undervoltage Lockout with Hysteresis
- Programmable State Controller

Corporate Headquarters
1300 Terra Bella Avenue,
Mountain View, CA 94043
Phone: (650) 968-9241
Fax: (650) 967-1590



TelCom
Semiconductor, Inc.

Analog & Mixed Signal Solutions

Literature: 1-800-888-9966 • www.telcom-semi.com

Order Your
1999 Data Book
Now!

